

INSTRUCTIONS:

1. The project report should be neatly typed.
2. Avoid using Abbreviations.
3. The text should be justified and typed in the Font style 'Times New Roman' and Font size '12'.
4. Heading and subheading should be bold.
5. The length of the report may be about 10 to 15 pages.

DON BOSCO INSTITUTE OF TECHNOLOGY



Skill Lab: C++ and Java Programming MINI PROJECT REPORT

On

**“Title of mini-project”
2021-22**

Submitted By:

Student_1: Jaipreet Singh	Student_1: 11
Student_2: Anto ridon	Student_2: 05
Student_3: Nadhanial Antony	Student_3: 16

Under the guidance of
Ms. Deepali Kayande

Mini Project Title : 4 BIT BINARY ADDER AND SUBTRACTOR

Institute Name : Don Bosco Institute of Technology.

**Institute Address : Premier Automobiles Road,
Kurla (West), Mumbai – 400070**

Department : EXTC

Class : 3rd SEM

Project Group Members :

	Names of students	Roll No.
1.	Jaipreet Singh	11
2.	Anto Ridon	05
3.	Nadhanial Antony	16
4.		
5.		

Date of Submission : 10/12/2021

Guide : Ms. Deepali Kayande

TABLE OF CONTENTS

SR. NO.	CONTENT	PAGE NO.
CHAPTER 1	INTRODUCTION	
CHAPTER 2	PROBLEM DEFINITION MODULES (IF ANY)	
CHAPTER 3	IMPLEMENTATION	
CHAPTER 4	RESULTS(SNAPSHOTS)	
CHAPTER 5	CONCLUSION	
CHAPTER 6	REFERENCES	

CHAPTER 1

INTRODUCTION

In Digital Circuits, A **Binary Adder-Subtractor** is one which is capable of both addition and subtraction of binary numbers in one circuit itself. The operation being performed depends upon the binary value the control signal holds. It is one of the components of the ALU (Arithmetic Logic Unit).


This Circuit Requires prerequisite knowledge of Exor Gate, Binary Addition and Subtraction, Full Adder.

Lets consider two 4-bit binary numbers A and B as inputs to the Digital Circuit for the operation with digits

A0 A1 A2 A3 for A

B0 B1 B2 B3 for B

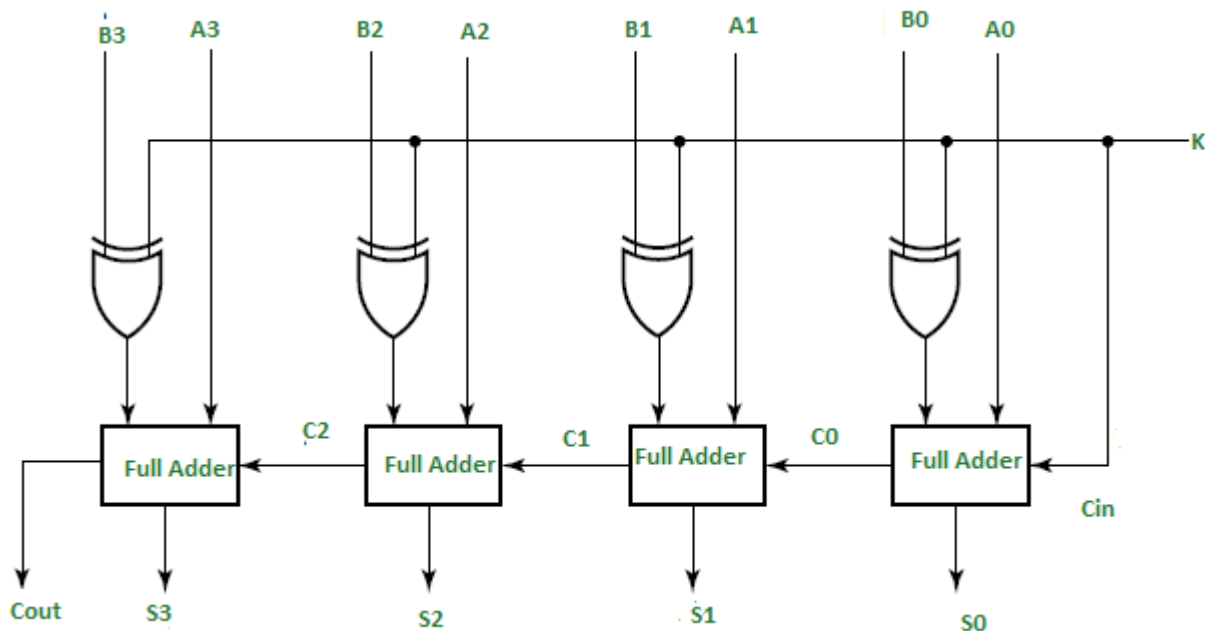The circuit consists of 4 full adders since we are performing operation on 4-bit numbers. There is a control line K that holds a binary value of either 0 or 1 which determines that the operation being carried out is addition or subtraction.



As shown in the figure, the first full adder has control line directly as its input(input carry Cin), The input A0 (The least significant bit of A) is directly input in the full adder. The third input is the exor of B0 and K. The two outputs produced are Sum/Difference (S0) and Carry (C0).

If the value of K (Control line) is 1, the output of B0(exor)K=B0'(Complement B0). Thus the operation would be $A+(B0')$. Now 2's complement subtraction for two

numbers A and B is given by $A+B'$. This suggests that when $K=1$, the operation being performed on the four bit numbers is subtraction.

Similarly If the Value of $K=0$, B_0 (exor) $K=B_0$. The operation is $A+B$ which is simple binary addition. This suggests that When $K=0$, the operation being performed on the four bit numbers is addition.

Then C_0 is serially passed to the second full adder as one of it's outputs. The sum/difference S_0 is recorded as the least significant bit of the sum/difference. A_1 , A_2 , A_3 are direct inputs to the second, third and fourth full adders. Then the third input is the B_1 , B_2 , B_3 EXORed with K to the second, third and fourth full adder respectively. The carry C_1 , C_2 are serially passed to the successive full adder as one of the inputs. C_3 becomes the total carry to the sum/difference. S_1 , S_2 , S_3 are recorded to form the result with S_0 .

For an n-bit binary adder-subtractor, we use n number of full adders.

Example:

Lets take two 3 bit numbers $A=010$ and $B=011$ and input them in the full adder with both values of control lines.

For $K=0$:

B_0 (exor) $K=B_0$ and $C_0=K=0$

Thus from first full adder

$= A_0+B_0$

$= 0+1$

$= 1,$

$S_0=1$

$C_1=0$

Similarly,

$S_1=0$ with $C_2=1$

$S_2=1$ and $C_2=0$

Thus,

$A = 010 = 2$

$B = 011 = 3$

Sum = $0101 = 5$

For $K=1$

$B_0(\text{exor})K=B_0'$ and $C_0=k=1$

Thus

$S_0=1$ and $C_1=0$

Similarly

$S_1=1$ and $C_2=0$

$S_2=1$ and $c_3=0$

Thus,

$A = 010 = 2$

$B = 011 = 3$

$\text{Sum}(\text{Difference}) = 1111 = -1$

Implementation: Our code

```
public class MyClass {  
    public static int get_adder(int value1,int value2){  
        // value 1 take care of addition  
        // value 2 take care of carry  
  
        int carry=0;  
        while(value2!=0){  
            carry = value1&value2;  
            value1 = (value1^value2);  
            value2=carry<<1;  
        }  
        int result = value1;  
        return result;  
    }  
    public static int get_substracter(int value1,int value2){  
        // 2's complement of value 2  
        // add value 1 and value 2  
        value2 = ~value2;  
        value2+=1;  
        return value1+value2;  
    }  
    public static void main(String args[]) {  
        int value1 = 13;  
        int value2 = 4;  
        String binary_value1 = get_binary_value(value1);  
        String binary_value2 = get_binary_value(value2);  
        System.out.println("Value 1-> "+value1+" " +"Binary->" + binary_value1+ " "+" Value  
2-> "+value2+ " "+" Binary-> " + binary_value2);  
        int addition = get_adder(value1,value2);  
        System.out.println("Ans after addition "+addition + " " + "Binary->  
"+get_binary_value(addition));  
        int subtraction = get_substracter(value1,value2);  
        System.out.println("Ans after subtraction "+subtraction + " " + "Binary->  
"+get_binary_value(subtraction));  
    }  
}
```




```

}
public static String get_binary_value(int value){
int len =0;
int temp = value;
String answer = "";
while(temp != 0){
    len+=1;
    temp>>=1;
}
temp = len;
while(temp!=0){
    int pointer = 1<<(len - temp);
    if ((pointer & value )==0){
        answer += "0";
    }
    else{
        answer += "1";
    }
    temp-=1;
}
String result="";
int space = 32-answer.length();
for(int i=0;i<space;i++){
    result+="0";
}
result+=answer;
return answer;
}
}

```

Output:

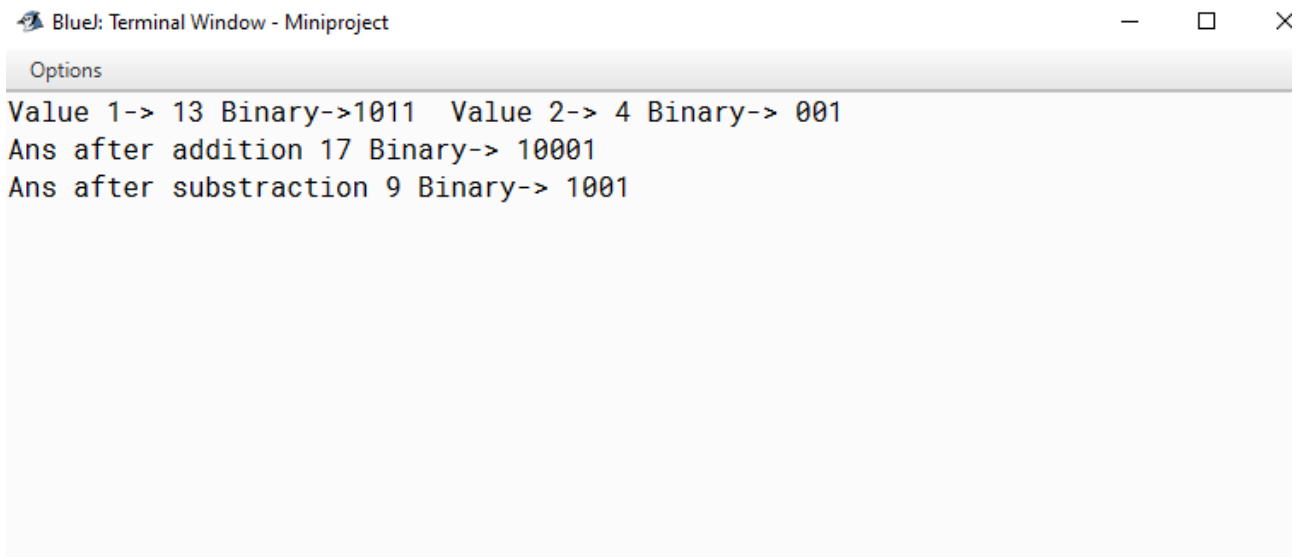

```
BlueJ: Terminal Window - Miniproject
Options
Value 1-> 13 Binary->1011  Value 2-> 4 Binary-> 001
Ans after addition 17 Binary-> 10001
Ans after subtraction 9 Binary-> 1001
```

Conclusion:

Here we conclude that we have find the 4 bit binary adder & subtractor and the code was verified and the output was obtained.

Blue J software was used for this implementation.

References:

- <https://www.geeksforgeeks.org/4-bit-binary-adder-subtractor/>
- <https://www.javatpoint.com/coa-binary-adder-subtractor>